

18007**B.C.A. Examination, June-2023****DIGITAL ELECTRONICS AND
COMPUTER ORGANISATION****(BCA-204)***Time : 3 Hours]**[Maximum Marks : 75*

Note: Attempt questions from **all** Sections as per instructions.

Section-A**(Very Short Answer Type Questions)**

Note : Attempt all the *five* questions. Each question carries 3 marks. Very short answer is required not exceeding 75 words. $5 \times 3 = 15$

1. Give the logic diagram and truth table of RS flip-flop. 3
2. Why RAM is used in computer? How static RAM is different from Dynamic RAM and where these RAMs are used in computer system? 3
3. Construct half adder circuit using basic gates. 3
4. State and prove De-Morgan theorem. 3

18007

[P. T. O.]

(2)

5. With logic diagram, characteristic table and the characteristic equation, explain the operation of a D Flip-Flop. 3

Section-B**(Short Answer Type Questions)**

Note: Attempt any *two* questions out of the following three questions. Each question carries 7.5 marks. Short answer is required not exceeding 200 words. $2 \times 7.5 = 15$

6. What are multiplexer and Demultiplexer? Also give the logical expression. $7\frac{1}{2}$
7. Draw and explain SISO, SIPO, PISO and PIPO shift registers with suitable example. $7\frac{1}{2}$
8. Implement following boolean function using multiplexers. $7\frac{1}{2}$

$$F(ABCD) = \Sigma(0, 1, 3, 4, 9, 15)$$

Section-C**(Descriptive Answer Type Questions)**

- Note:** Attempt any *three* questions out of the following five questions. Each question carries 15 marks. Answer is required in detail. $3 \times 15 = 45$
9. Explain cache memory and cache initialization. Give the significance of cache memory.

18007

(3)

A two way set associative cache memory uses block of four words. The cache can accommodate a total of 2048 words from the main memory. The main memory size is $128K \times 32$

- (a) Formulate all pertinent information required to construct the cache memory.
- (b) What is the size of cache memory? 15
- 10. Design a synchronous sequential circuit with 2 inputs T and C. The output attains a value of 1 when $T = 1$ and C moves from 1 to 0. Otherwise output is 0. 15
- 11. What is decoder? Draw the circuit of a 2 to 4 decoder and explain its functions. 15
- 12. Explain the difference between all of the following- 15
 - (a) Volatile and Non-Volatile memory
 - (b) Static and Dynamic memory
 - (c) Sequential and Random Access memory
 - (d) Magnetic and Semi-Conductor memory
 - (e) Sum of Product (SOP) and Product of Sum (POS)
- 13. Design an 32×8 memory RAM chip using 16×4 memory chips. 15